

Міністерство освіти і науки України
Національний університет «Львівська політехніка»

Кафедра ЕОМ



Звіт

до лабораторної роботи № 3

з дисципліни «Моделювання комп'ютерних систем»
на тему:

«Поведінковий опис цифрового автомата Перевірка роботи автомата за
допомогою стенда Elbert V2 – Spartan 3A FPGA»

Варіант №2

Виконав:
ст. гр. КІ-201
Бовтач О.М
Прийняв:
Козак Н. Б.

Львів 2024

Мета роботи: На базі стенда реалізувати цифровий автомат для обчислення значення виразів.

Виконання роботи:

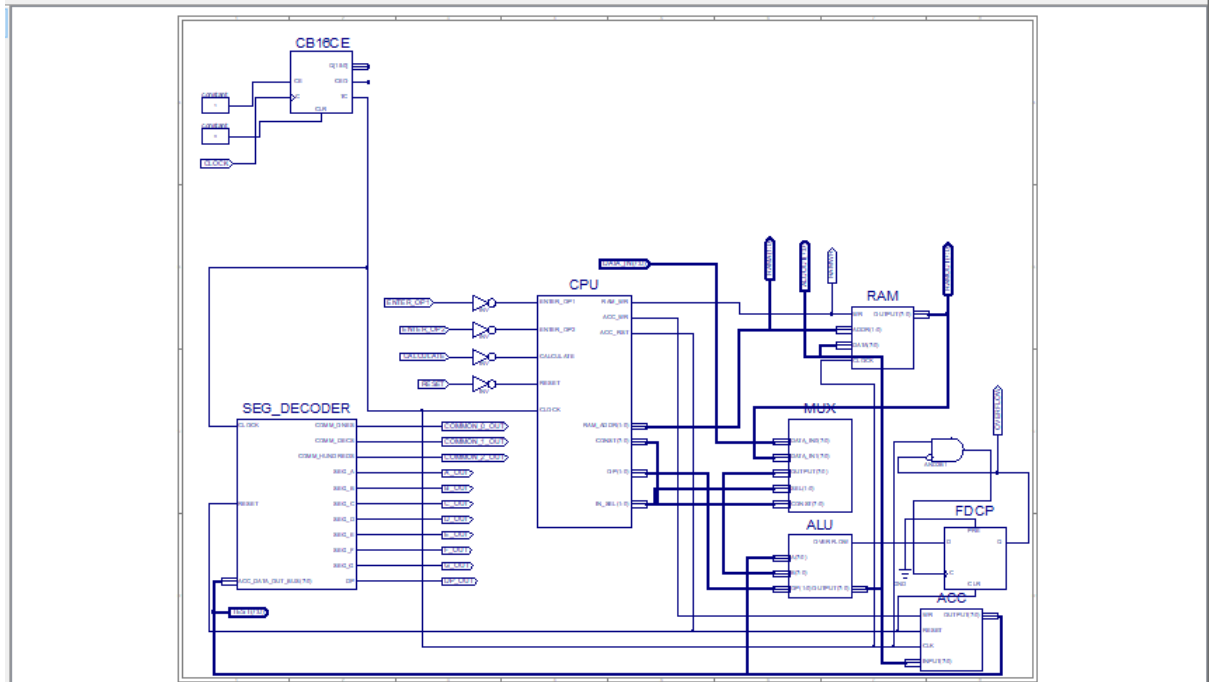


Рис. 1 – Top Level

Файл ACC.vhd

```
1. -----
2. -- Company:
3. -- Engineer:
4. --
5. -- Create Date:    17:16:45 04/29/2024
6. -- Design Name:
7. -- Module Name:    ACC - Behavioral
8. -- Project Name:
9. -- Target Devices:
10. -- Tool versions:
11. -- Description:
12. --
13. -- Dependencies:
14. --
15. -- Revision:
16. -- Revision 0.01 - File Created
17. -- Additional Comments:
18. --
19. -----
20. library IEEE;
21. use IEEE.STD_LOGIC_1164.ALL;
22.
23. -- Uncomment the following library declaration if using
24. -- arithmetic functions with Signed or Unsigned values
25. --use IEEE.NUMERIC_STD.ALL;
26.
27. -- Uncomment the following library declaration if instantiating
28. -- any Xilinx primitives in this code.
29. --library UNISIM;
```

```

30. --use UNISIM.VComponents.all;
31.
32. entity ACC is
33.     Port ( WR      : in  STD_LOGIC;
34.           RESET   : in  STD_LOGIC;
35.           CLK      : in  STD_LOGIC;
36.           INPUT    : in  STD_LOGIC_VECTOR (7 downto 0);
37.           OUTPUT   : out STD_LOGIC_VECTOR (7 downto 0));
38. end ACC;
39.
40. architecture ACC_arch of ACC is
41.     signal DATA : STD_LOGIC_VECTOR (7 downto 0);
42. begin
43.     process (CLK)
44.     begin
45.         if rising_edge(CLK) then
46.             if RESET = '1' then
47.                 DATA <= (others => '0');
48.             elsif WR = '1' then
49.                 DATA <= INPUT;
50.             end if;
51.         end if;
52.     end process;
53.
54.
55.     OUTPUT <= DATA;
56.
57. end ACC_arch;

```

Файл ALU.vhd

```

1. - Company:
2. -- Engineer:
3. --
4. -- Create Date:    11:09:43 05/07/2024
5. -- Design Name:
6. -- Module Name:    C:/Users/User/Documents/Lab_3_v6/ACCTest.vhd
7. -- Project Name:   Lab_3_Example
8. -- Target Device:
9. -- Tool versions:
10. -- Description:
11. --
12. -- VHDL Test Bench Created by ISE for module: ACC
13. --
14. -- Dependencies:
15. --
16. -- Revision:
17. -- Revision 0.01 - File Created
18. -- Additional Comments:
19. --
20. -- Notes:
21. -- This testbench has been automatically generated using types std_logic and
22. -- std_logic_vector for the ports of the unit under test.  Xilinx recommends
23. -- that these types always be used for the top-level I/O of a design in order
24. -- to guarantee that the testbench will bind correctly to the post-implementation
25. -- simulation model.
26. -----
27. LIBRARY ieee;
28. USE ieee.std_logic_1164.ALL;
29.
30. -- Uncomment the following library declaration if using
31. -- arithmetic functions with Signed or Unsigned values
32. --USE ieee.numeric_std.ALL;
33.
34. ENTITY ACCTest IS

```

```

35. END ACCTest;
36.
37. ARCHITECTURE behavior OF ACCTest IS
38.
39.     -- Component Declaration for the Unit Under Test (UUT)
40.
41.     COMPONENT ACC
42.     PORT(
43.         WR : IN  std_logic;
44.         RESET : IN  std_logic;
45.         CLK : IN  std_logic;
46.         INPUT : IN  std_logic_vector(7 downto 0);
47.         OUTPUT : OUT  std_logic_vector(7 downto 0)
48.     );
49.     END COMPONENT;
50.
51.
52.     --Inputs
53.     signal WR : std_logic := '0';
54.     signal RESET : std_logic := '0';
55.     signal CLK : std_logic := '0';
56.     signal INPUT : std_logic_vector(7 downto 0) := (others => '0');
57.
58.     --Outputs
59.     signal OUTPUT : std_logic_vector(7 downto 0);
60.
61.     -- Clock period definitions
62.     constant CLKP: time := 2 ps;
63.
64. BEGIN
65.
66.     -- Instantiate the Unit Under Test (UUT)
67.     uut: ACC PORT MAP (
68.         WR => WR,
69.         RESET => RESET,
70.         CLK => CLK,
71.         INPUT => INPUT,
72.         OUTPUT => OUTPUT
73.     );
74.
75.     -- Clock process definitions
76.     CLK_process :process
77.     begin
78.         CLK <= '0';
79.         wait for CLKP/2;
80.         CLK <= '1';
81.         wait for CLKP/2;
82.     end process;
83.
84.
85.     -- Stimulus process
86.     stim_proc: process
87.     begin
88.         RESET <= '1';
89.         wait for 4 * CLKP;
90.         RESET <= '0';
91.         WR <= '0';
92.         INPUT <= "00001111";
93.         wait for CLKP;
94.         assert OUTPUT = "00000000" severity failure;
95.         WR <= '1';
96.         wait for CLKP;
97.         assert OUTPUT = "00001111" severity failure;
98.         INPUT <= "11110000";
99.         wait for CLKP;
100.         assert OUTPUT = "11110000" severity failure;

```

```

101.
102.         wait;
103.         end process;
104.
105. END;

```

Файл CPU.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4.
5. entity CPU is
6.     port( ENTER_OP1 : IN STD_LOGIC;
7.           ENTER_OP2 : IN STD_LOGIC;
8.           CALCULATE : IN STD_LOGIC;
9.           RESET : IN STD_LOGIC;
10.          CLOCK : IN STD_LOGIC;
11.          RAM_WR : OUT STD_LOGIC;
12.          RAM_ADDR : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
13.          CONST : OUT STD_LOGIC_VECTOR(7 DOWNTO 0);
14.          ACC_WR : OUT STD_LOGIC;
15.          ACC_RST : OUT STD_LOGIC;
16.          IN_SEL : OUT STD_LOGIC_VECTOR(1 DOWNTO 0);
17.          OP : OUT STD_LOGIC_VECTOR(1 DOWNTO 0));
18. end CPU;
19.
20. architecture CPU_arch of CPU is
21.
22. type STATE_TYPE is (RST, IDLE, LOAD_OP1, LOAD_OP2, RUN_CALC0, RUN_CALC1,
23.                     RUN_CALC2, RUN_CALC3, RUN_CALC4, FINISH);
24. signal CUR_STATE : STATE_TYPE;
25. signal NEXT_STATE : STATE_TYPE;
26. begin
27.     SYNC_PROC: process (CLOCK)
28.     begin
29.         if (rising_edge(CLOCK)) then
30.             if (RESET = '1') then
31.                 CUR_STATE <= RST;
32.             else
33.                 CUR_STATE <= NEXT_STATE;
34.             end if;
35.         end if;
36.     end process;
37.
38.
39.     NEXT_STATE_DECODE: process (CLOCK, ENTER_OP1, ENTER_OP2, CALCULATE)
40.     begin
41.         NEXT_STATE <= CUR_STATE;
42.
43.         case(CUR_STATE) is
44.             when RST =>
45.                 NEXT_STATE <= IDLE;
46.             when IDLE =>
47.                 if (ENTER_OP1 = '1') then
48.                     NEXT_STATE <= LOAD_OP1;
49.                 elsif (ENTER_OP2 = '1') then
50.                     NEXT_STATE <= LOAD_OP2;
51.                 elsif (CALCULATE = '1') then
52.                     NEXT_STATE <= RUN_CALC0;
53.                 else
54.                     NEXT_STATE <= IDLE;
55.                 end if;

```

```

56.         when LOAD_OP1 =>
57.             NEXT_STATE <= IDLE;
58.         when LOAD_OP2 =>
59.             NEXT_STATE <= IDLE;
60.         when RUN_CALC0 =>
61.             NEXT_STATE <= RUN_CALC1;
62.         when RUN_CALC1 =>
63.             NEXT_STATE <= RUN_CALC2;
64.         when RUN_CALC2 =>
65.             NEXT_STATE <= RUN_CALC3;
66.         when RUN_CALC3 =>
67.             NEXT_STATE <= RUN_CALC4;
68.         when RUN_CALC4 =>
69.             NEXT_STATE <= FINISH;
70.         when FINISH =>
71.             NEXT_STATE <= FINISH;
72.         when others =>
73.             NEXT_STATE <= IDLE;
74.         end case;
75.     end process;
76.
77.     OUTPUT_DECODE: process (CUR_STATE)
78.     begin
79.         case (CUR_STATE) is
80.             when RST =>
81.                 RAM_WR <= '0';
82.                 RAM_ADDR <= "00";
83.                 CONST <= "00000000";
84.                 ACC_WR <= '0';
85.                 ACC_RST <= '1';
86.                 IN_SEL <= "00";
87.                 OP <= "00";
88.             when LOAD_OP1 =>
89.                 RAM_WR <= '1';
90.                 RAM_ADDR <= "00";
91.                 CONST <= "00000000";
92.                 ACC_WR <= '0';
93.                 ACC_RST <= '1';
94.                 IN_SEL <= "00";
95.                 OP <= "00";
96.             when LOAD_OP2 =>
97.                 RAM_WR <= '1';
98.                 RAM_ADDR <= "01";
99.                 CONST <= "00000000";
100.                 ACC_WR <= '0';
101.                 ACC_RST <= '1';
102.                 IN_SEL <= "00";
103.                 OP <= "00";
104.             when RUN_CALC0 =>
105.                 RAM_WR <= '0';
106.                 RAM_ADDR <= "00";
107.                 CONST <= "00000000";
108.                 ACC_WR <= '1';
109.                 ACC_RST <= '0';
110.                 IN_SEL <= "01";
111.                 OP <= "00";
112.             when RUN_CALC1 =>
113.                 RAM_WR <= '0';
114.                 RAM_ADDR <= "01";
115.                 CONST <= "00000000";
116.                 ACC_WR <= '1';
117.                 ACC_RST <= '0';
118.                 IN_SEL <= "01";
119.                 OP <= "11";
120.             when RUN_CALC2 =>
121.                 RAM_WR <= '0';

```

```

122.             RAM_ADDR <= "01";
123.             CONST <= "00000000";
124.             ACC_WR <= '1';
125.             ACC_RST <= '0';
126.             IN_SEL <= "01";
127.             OP <= "01";
128.         when RUN_CALC3 =>
129.             RAM_WR <= '0';
130.             RAM_ADDR <= "01";
131.             CONST <= "00001010";
132.             ACC_WR <= '1';
133.             ACC_RST <= '0';
134.             IN_SEL <= "10";
135.             OP <= "01";
136.         when RUN_CALC4 =>
137.             RAM_WR <= '0';
138.             RAM_ADDR <= "00";
139.             CONST <= "00000011";
140.             ACC_WR <= '1';
141.             ACC_RST <= '0';
142.             IN_SEL <= "10";
143.             OP <= "10";
144.         when IDLE =>
145.             RAM_WR <= '0';
146.             RAM_ADDR <= "00";
147.             CONST <= "00000000";
148.             ACC_WR <= '0';
149.             ACC_RST <= '0';
150.             IN_SEL <= "00";
151.             OP <= "00";
152.         when others =>
153.             RAM_WR <= '0';
154.             RAM_ADDR <= "00";
155.             CONST <= "00000000";
156.             ACC_WR <= '0';
157.             ACC_RST <= '0';
158.             IN_SEL <= "00";
159.             OP <= "00";
160.         end case;
161.     end process;
162. end CPU_arch;

```

Файл MUX.vhd

```

1. library IEEE;
2. use IEEE.STD_LOGIC_1164.ALL;
3.
4. entity MUX is
5.     PORT(
6.         SEL: in STD_LOGIC_VECTOR(1 downto 0);
7.         CONST: in STD_LOGIC_VECTOR(7 downto 0);
8.         --CONST1: in STD_LOGIC_VECTOR()
9.         DATA_IN0: in STD_LOGIC_VECTOR(7 downto 0);
10.        DATA_IN1: in STD_LOGIC_VECTOR(7 downto 0);
11.        OUTPUT: out STD_LOGIC_VECTOR(7 downto 0)
12.    );
13. end MUX;
14.
15. architecture Behavioral of MUX is
16. begin
17.     process (SEL, DATA_IN0, DATA_IN1, CONST)
18.     begin
19.         if (SEL = "00") then
20.             OUTPUT <= DATA_IN0;
21.         elsif (SEL = "01") then

```

```

22.             OUTPUT <= DATA_IN1;
23.             else
24.             OUTPUT <= CONST;
25.             end if;
26.         end process;
27. end Behavioral;

```

Файл RAM.vhd

```

1. -----
2. -- Company:
3. -- Engineer:
4. --
5. -- Create Date:    02:03:24 04/21/2024
6. -- Design Name:
7. -- Module Name:    RAM - RAM_arch
8. -- Project Name:
9. -- Target Devices:
10. -- Tool versions:
11. -- Description:
12. --
13. -- Dependencies:
14. --
15. -- Revision:
16. -- Revision 0.01 - File Created
17. -- Additional Comments:
18. --
19. -----
20. library IEEE;
21. use IEEE.STD_LOGIC_1164.ALL;
22. use IEEE.NUMERIC_STD.ALL;
23. use IEEE.STD_LOGIC_UNSIGNED.ALL;
24.
25.
26. entity RAM is
27. port(
28.         WR : IN STD_LOGIC;
29.         ADDR : IN STD_LOGIC_VECTOR(1 DOWNTO 0);
30.         DATA : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
31.         CLOCK: IN STD_LOGIC;
32.         OUTPUT : OUT STD_LOGIC_VECTOR(7 DOWNTO 0)
33.     );
34. end RAM;
35.
36. architecture RAM_arch of RAM is
37. type ram_type is array (3 downto 0) of STD_LOGIC_VECTOR(7 downto 0);
38. signal UNIT : ram_type;
39.
40. begin
41. process(ADDR, CLOCK, UNIT)
42. begin
43.     if(rising_edge(CLOCK)) then
44.         if (WR = '1') then
45.             UNIT(conv_integer(ADDR)) <= DATA;
46.         end if;
47.     end if;
48.     OUTPUT <= UNIT(conv_integer(ADDR));
49. end process;
50. end RAM_arch;

```


Файл SEG_DECODER.vhd

```
1. -----
2. -
3. -- Company:
4. -- Engineer:
5. -- Create Date:    02:34:19 04/21/2024
6. -- Design Name:
7. -- Module Name:    BIN_TO_BCD - Behavioral
8. -- Project Name:
9. -- Target Devices:
10. -- Tool versions:
11. -- Description:
12. --
13. -- Dependencies:
14. --
15. -- Revision:
16. -- Revision 0.01 - File Created
17. -- Additional Comments:
18. --
19. -----
20. -
21. library IEEE;
22. use IEEE.STD_LOGIC_1164.ALL;
23. use IEEE.STD_LOGIC_ARITH.ALL;
24. use IEEE.STD_LOGIC_UNSIGNED.ALL;
25.
26. entity SEG_DECODER is
27.     port( CLOCK : IN STD_LOGIC;
28.           RESET : IN STD_LOGIC;
29.           ACC_DATA_OUT_BUS : IN STD_LOGIC_VECTOR(7 DOWNTO 0);
30.           COMM_ONES       : OUT STD_LOGIC;
31.           COMM_DECS       : OUT STD_LOGIC;
32.           COMM_HUNDREDS   : OUT STD_LOGIC;
33.           SEG_A           : OUT STD_LOGIC;
34.           SEG_B           : OUT STD_LOGIC;
35.           SEG_C           : OUT STD_LOGIC;
36.           SEG_D           : OUT STD_LOGIC;
37.           SEG_E           : OUT STD_LOGIC;
38.           SEG_F           : OUT STD_LOGIC;
39.           SEG_G           : OUT STD_LOGIC;
40.           DP              : OUT STD_LOGIC);
41. end SEG_DECODER;
42.
43. architecture Behavioral of SEG_DECODER is
44.
45.     signal ONES_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
46.     signal DECS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0001";
47.     signal HONDREDS_BUS : STD_LOGIC_VECTOR(3 downto 0) := "0000";
48.
49. begin
50.     BIN_TO_BCD : process (ACC_DATA_OUT_BUS)
51.     variable hex_src : STD_LOGIC_VECTOR(7 downto 0) ;
52.     variable bcd      : STD_LOGIC_VECTOR(11 downto 0) ;
53.     begin
54.         bcd      := (others => '0') ;
55.         hex_src  := ACC_DATA_OUT_BUS;
56.
57.         for i in hex_src'range loop
58.             if bcd(3 downto 0) > "0100" then
59.                 bcd(3 downto 0) := bcd(3 downto 0) + "0011" ;
60.             end if ;
61.             if bcd(7 downto 4) > "0100" then
```

```

62.         bcd(7 downto 4) := bcd(7 downto 4) + "0011" ;
63.     end if ;
64.     if bcd(11 downto 8) > "0100" then
65.         bcd(11 downto 8) := bcd(11 downto 8) + "0011" ;
66.     end if ;
67.
68.     bcd := bcd(10 downto 0) & hex_src(hex_src'left) ; -- shift bcd + 1
new entry
69.     hex_src := hex_src(hex_src'left - 1 downto hex_src'right) & '0' ; --
shift src + pad with 0
70.     end loop ;
71.
72.     HONDREDS_BUS      <= bcd (11 downto 8);
73.     DECS_BUS          <= bcd (7  downto 4);
74.     ONES_BUS          <= bcd (3  downto 0);
75.
76. end process BIN_TO_BCD;
77.
78.     INDICATE : process(CLOCK)
79.         type DIGIT_TYPE is (ONES, DECS, HUNDREDS);
80.
81.         variable CUR_DIGIT      : DIGIT_TYPE := ONES;
82.         variable DIGIT_VAL      : STD_LOGIC_VECTOR(3 downto 0) := "0000";
83.         variable DIGIT_CTRL     : STD_LOGIC_VECTOR(6 downto 0) :=
"0000000";
84.         variable COMMONS_CTRL  : STD_LOGIC_VECTOR(2 downto 0) := "000";
85.
86.     begin
87.         if (rising_edge(CLOCK)) then
88.             if(RESET = '0') then
89.                 case CUR_DIGIT is
90.                     when ONES =>
91.                         DIGIT_VAL := ONES_BUS;
92.                         CUR_DIGIT := DECS;
93.                         COMMONS_CTRL := "001";
94.                     when DECS =>
95.                         DIGIT_VAL := DECS_BUS;
96.                         CUR_DIGIT := HUNDREDS;
97.                         COMMONS_CTRL := "010";
98.                     when HUNDREDS =>
99.                         DIGIT_VAL := HONDREDS_BUS;
100.                        CUR_DIGIT := ONES;
101.                        COMMONS_CTRL :=
"100";
102.
103.                        when others =>
DIGIT_VAL :=
ONES_BUS;
104.
CUR_DIGIT := ONES;
105.
COMMONS_CTRL :=
"000";
106.
end case;
107.
108.         case DIGIT_VAL is
--
109.             when "0000" => DIGIT_CTRL :=
"1111110";
110.             when "0001" => DIGIT_CTRL :=
"0110000";
111.             when "0010" => DIGIT_CTRL :=
"1101101";
112.             when "0011" => DIGIT_CTRL :=
"1111001";
113.             when "0100" => DIGIT_CTRL :=
"0110011";
114.             when "0101" => DIGIT_CTRL :=
"1011011";

```

```

115.                                     when "0110" => DIGIT_CTRL :=
    "1011111";
116.                                     when "0111" => DIGIT_CTRL :=
    "1110000";
117.                                     when "1000" => DIGIT_CTRL :=
    "1111111";
118.                                     when "1001" => DIGIT_CTRL :=
    "1111011";
119.                                     when others => DIGIT_CTRL :=
    "0000000";
120.                                     end case;
121.     else
122.         DIGIT_VAL := ONES_BUS;
123.         CUR_DIGIT := ONES;
124.         COMMONS_CTRL := "000";
125.     end if;
126.
127.     COMM_ONES      <= not COMMONS_CTRL(0);
128.     COMM_DECS      <= not COMMONS_CTRL(1);
129.     COMM_HUNDREDS <= not COMMONS_CTRL(2);
130.
131.     SEG_A <= not DIGIT_CTRL(6);
132.     SEG_B <= not DIGIT_CTRL(5);
133.     SEG_C <= not DIGIT_CTRL(4);
134.     SEG_D <= not DIGIT_CTRL(3);
135.     SEG_E <= not DIGIT_CTRL(2);
136.     SEG_F <= not DIGIT_CTRL(1);
137.     SEG_G <= not DIGIT_CTRL(0);
138.     DP      <= '1';
139.
140.                                     end if;
141.     end process INDICATE;
142.
143. end Behavioral;

```

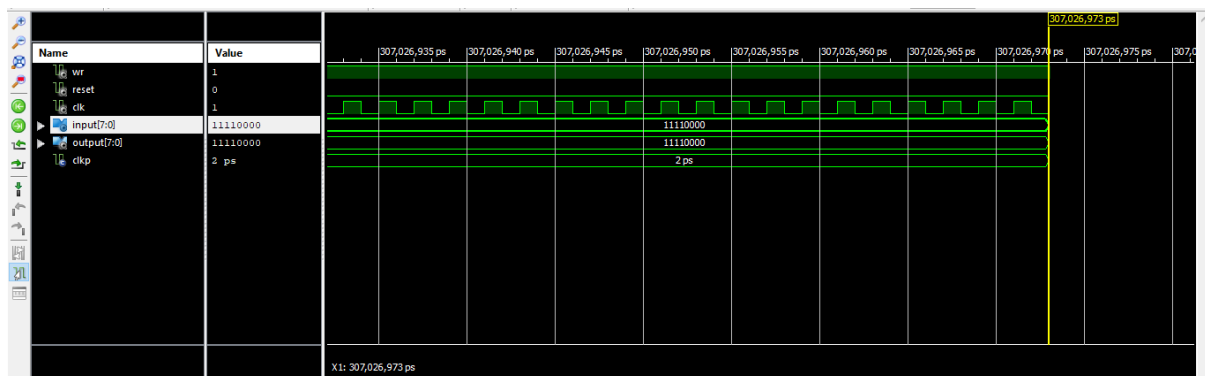


Рис. 2 – Часова діаграма ACC

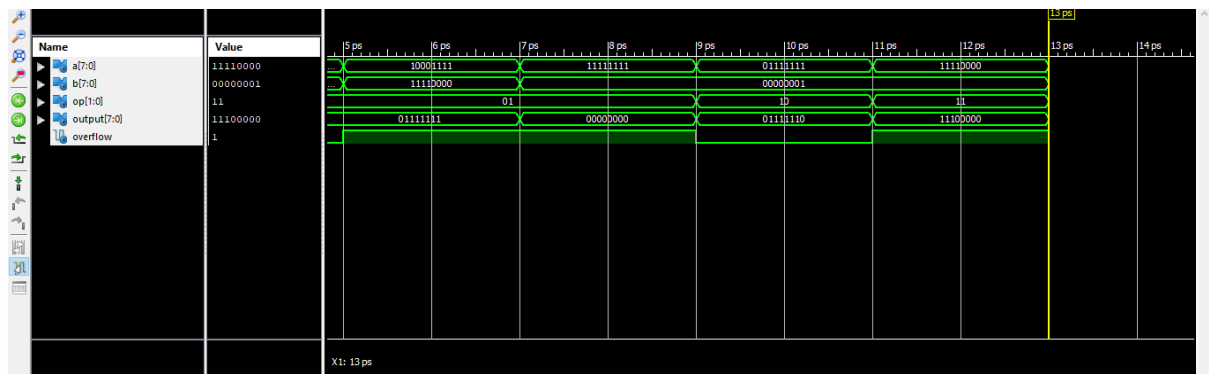


Рис. 3 – Часова діаграма ALU

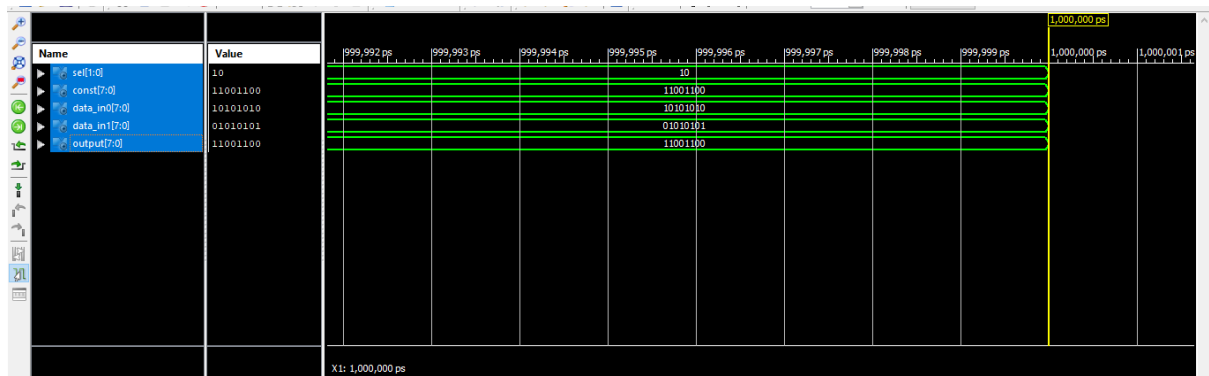


Рис. 4 – Часова діаграма MUX

 


Рис. 5 – Часова діаграма RAM

 


Рис 6. – Часова діграма SEG_DECODER

 


Рис. 7. – Часова діаграма TopLevel

Файл TopLevelTest.vhd

```

1. -- Vhdl test bench created from schematic
   C:\Users\User\Documents\Lab_3\TopLevel.sch - Mon Apr 29 19:00:56 2024
2. --
3. -- Notes:
4. -- 1) This testbench template has been automatically generated using types
5. -- std_logic and std_logic_vector for the ports of the unit under test.
6. -- Xilinx recommends that these types always be used for the top-level
7. -- I/O of a design in order to guarantee that the testbench will bind
8. -- correctly to the timing (post-route) simulation model.
9. -- 2) To use this template as your testbench, change the filename to any
10. -- name of your choice with the extension .vhd, and use the "Source->Add"
11. -- menu in Project Navigator to import the testbench. Then
12. -- edit the user defined section below, adding code to generate the
13. -- stimulus for your design.
14. --
15. LIBRARY ieee;
16. USE ieee.std_logic_1164.ALL;
17. USE ieee.numeric_std.ALL;
18. LIBRARY UNISIM;
19. USE UNISIM.vcomponents.ALL;
20. ENTITY TopLevel_TopLevel_sch_tb IS
21. END TopLevel_TopLevel_sch_tb;
22. ARCHITECTURE behavioral OF TopLevel_TopLevel_sch_tb IS
23.
24.     COMPONENT TopLevel
25.     PORT( CLOCK :      IN      STD_LOGIC;
26.           RESET       :      IN      STD_LOGIC;
27.           ENTER_OP1   :      IN      STD_LOGIC;
28.           ENTER_OP2   :      IN      STD_LOGIC;
29.           CALCULATE    :      IN      STD_LOGIC;
30.           DATA_IN     :      IN      STD_LOGIC_VECTOR (7 DOWNTO 0);
31.           COMMON_0_OUT :      OUT     STD_LOGIC;
32.           COMMON_1_OUT :      OUT     STD_LOGIC;
33.           COMMON_2_OUT :      OUT     STD_LOGIC;
34.           TEST         :      OUT     STD_LOGIC_VECTOR(7 downto 0);
35.           A_OUT        :      OUT     STD_LOGIC;
36.           B_OUT        :      OUT     STD_LOGIC;
37.           C_OUT        :      OUT     STD_LOGIC;
38.           D_OUT        :      OUT     STD_LOGIC;
39.           E_OUT        :      OUT     STD_LOGIC;
40.           F_OUT        :      OUT     STD_LOGIC;
41.           G_OUT        :      OUT     STD_LOGIC;
42.           DP_OUT       :      OUT     STD_LOGIC;
43.           RAMOUT       :      OUT     STD_LOGIC_VECTOR(7 downto 0);
44.           ALUOUT       :      OUT     STD_LOGIC_VECTOR(7 downto 0);
45.           RAMA         :      OUT     STD_LOGIC_VECTOR(1 downto 0);
46.           RAMWR        :      OUT     STD_LOGIC;

```

```

47.         OVERFLOW      :      OUT      STD_LOGIC);
48.     END COMPONENT;
49.
50.     SIGNAL CLOCK        :      STD_LOGIC := '0';
51.     SIGNAL RESET        :      STD_LOGIC;
52.     SIGNAL ENTER_OP1    :      STD_LOGIC;
53.     SIGNAL ENTER_OP2    :      STD_LOGIC;
54.     SIGNAL CALCULATE     :      STD_LOGIC;
55.     SIGNAL DATA_IN      :      STD_LOGIC_VECTOR (7 DOWNT0 0);
56.     SIGNAL COMMON_0_OUT  :      STD_LOGIC;
57.     SIGNAL COMMON_1_OUT  :      STD_LOGIC;
58.     SIGNAL COMMON_2_OUT  :      STD_LOGIC;
59.     SIGNAL A_OUT         :      STD_LOGIC;
60.     SIGNAL B_OUT         :      STD_LOGIC;
61.     SIGNAL C_OUT         :      STD_LOGIC;
62.     SIGNAL D_OUT         :      STD_LOGIC;
63.     SIGNAL E_OUT         :      STD_LOGIC;
64.     SIGNAL F_OUT         :      STD_LOGIC;
65.     SIGNAL G_OUT         :      STD_LOGIC;
66.     SIGNAL DP_OUT        :      STD_LOGIC;
67.     SIGNAL OVERFLOW      :      STD_LOGIC;
68.     SIGNAL TEST: STD_LOGIC_VECTOR(7 downto 0);
69.     SIGNAL TEST2: STD_LOGIC_VECTOR(7 downto 0);
70.     signal RAMOUT: STD_LOGIC_VECTOR(7 downto 0);
71.     signal ALUOUT: STD_LOGIC_VECTOR(7 downto 0);
72.     signal RAMA: STD_LOGIC_VECTOR(1 downto 0);
73.     signal RAMWR: STD_LOGIC;
74.
75. --     constant CLOCK_period : time := 166ns;
76.     constant CLKP: time := 12ms;--24ms;
77.
78. BEGIN
79.
80.     UUT: TopLevel PORT MAP(
81.         CLOCK => CLOCK,
82.         RESET => RESET,
83.         ENTER_OP1 => ENTER_OP1,
84.         ENTER_OP2 => ENTER_OP2,
85.         CALCULATE => CALCULATE,
86.         DATA_IN => DATA_IN,
87.         COMMON_0_OUT => COMMON_0_OUT,
88.         COMMON_1_OUT => COMMON_1_OUT,
89.         COMMON_2_OUT => COMMON_2_OUT,
90.         A_OUT => A_OUT,
91.         B_OUT => B_OUT,
92.         C_OUT => C_OUT,
93.         D_OUT => D_OUT,
94.         E_OUT => E_OUT,
95.         F_OUT => F_OUT,
96.         G_OUT => G_OUT,
97.         DP_OUT => DP_OUT,
98.         OVERFLOW => OVERFLOW,
99.         TEST => TEST,
100.         RAMOUT => RAMOUT,
101.         ALUOUT => ALUOUT,
102.         RAMA => RAMA,
103.         RAMWR => RAMWR
104.     );
105.
106.     CLOCK_process: process
107.     begin
108.         CLOCK <= '0';
109.         wait for 83ns;
110.         CLOCK <= '1';
111.         wait for 83ns;
112.     end process;

```

```

113.
114.      -- *** Test Bench - User Defined Section ***
115.      tb : PROCESS
116.      BEGIN
117.          lp1: for i in 4 to 4 loop
118.              lp2: for j in 2 to 2 loop
119.                  TEST2 <=
std_logic_vector(to_unsigned(to_integer(signed(std_logic_vector(to_unsigned(j,
8)) or std_logic_vector(to_unsigned(i, 8)))) + j + 10 - 3, 8));
120.                  ENTER_OP1 <= '1';
121.                  ENTER_OP2 <= '1';
122.                  CALCULATE <= '1';
123.                  DATA_IN <= (others => '0');
124.                  RESET <= '0';
125.                  wait for CLKP;
126.                  RESET <= '1';
127.                  wait for CLKP;
128.                  DATA_IN <= std_logic_vector(to_unsigned(i,
8)); -- A
129.                  ENTER_OP1 <= '0';
130.                  wait for CLKP;
131.                  ENTER_OP1 <= '1';
132.                  wait for CLKP;
133.                  DATA_IN <= std_logic_vector(to_unsigned(j,
8)); -- B
134.                  ENTER_OP2 <= '0';
135.                  wait for CLKP;
136.                  ENTER_OP2 <= '1';
137.                  wait for CLKP;
138.                  CALCULATE <= '0'; -- START CALCULATION
139.                  wait for CLKP* 7;
140.                  assert TEST = TEST2 severity FAILURE;
141.                  wait for CLKP;
142.              end loop;
143.          end loop;
144.
145.          WAIT; -- will wait forever
146.      END PROCESS;
147.      -- *** End Test Bench - User Defined Section ***
148.
149.  END;

```

 


Рис.8 – 7-сегментний індикатор

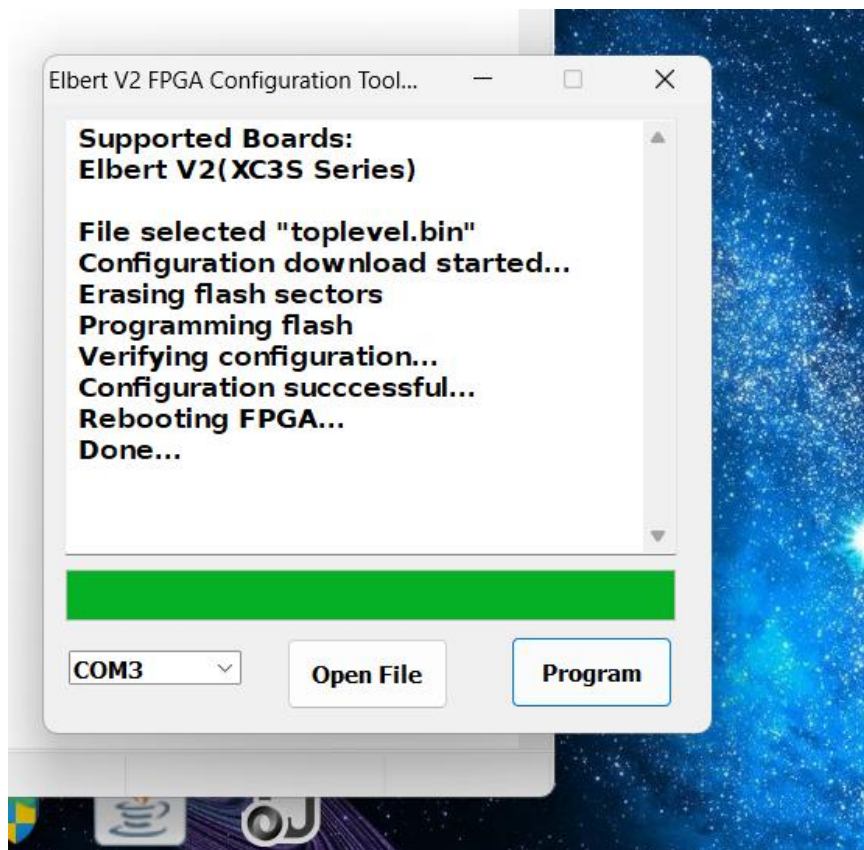


Рис.9 – Успішна прошивка

Висновок: Виконуючи дану лабораторну роботу я навчився реалізовувати цифровий автомат для обчислення значення виразів використовуючи засоби VHDL.